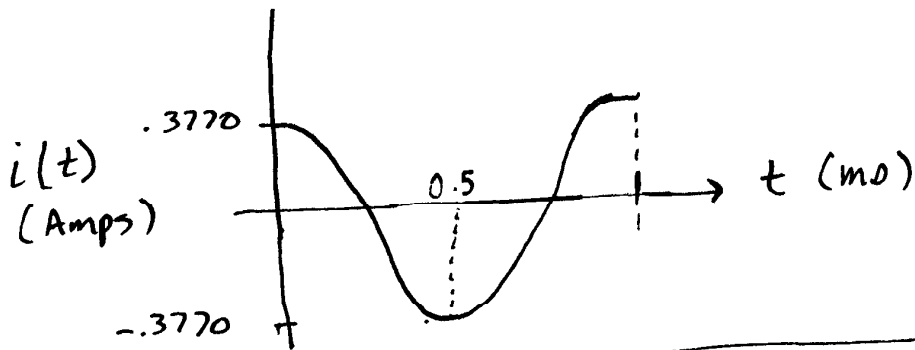


6.14. Note that $v(t) = 10 \sin(2\pi \cdot 1000 t)$

$$i(t) = C \frac{dv(t)}{dt} = (6 \times 10^{-6})(10)(2\pi \cdot 1000) \cdot \cos(2\pi \cdot 1000 t)$$

$$= 0.3770 \cos(2\pi \cdot 1000 t) \text{ A}$$




6.15 Using $v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx$

for $t = 0 \dots 4 \text{ ms}$, $v(t) = \frac{1}{200e^{-6}} \int_0^t \frac{5}{4} x dx$

$$= \frac{1}{2e^{-4}} \left(\frac{5}{4} \right) \frac{x^2}{2} \Big|_0^t$$

$$= \frac{5}{1.6e^{-3}} t^2 = 3125 t^2$$

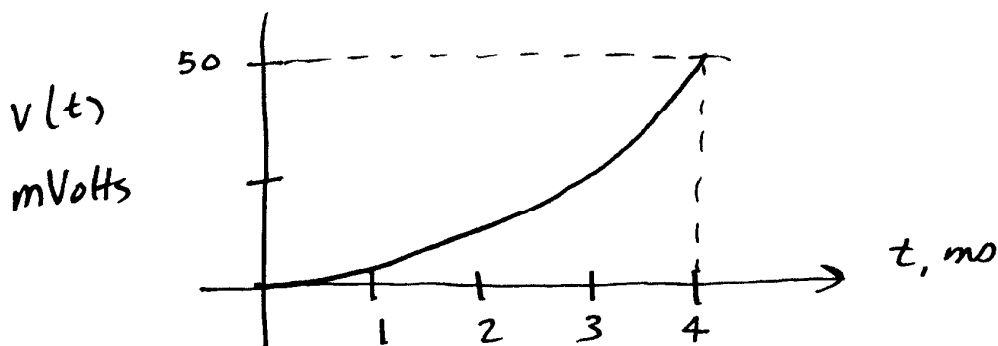


$$6.16 \quad \frac{di}{dt} = \frac{200 \text{ mA}}{4 \text{ ms}} = 50 \frac{\text{A}}{\text{s}}$$

$$\text{Since } V = L \frac{di}{dt}$$

$$100 \text{ mV} = L \cdot 50 \text{ A/s}$$

$$\underline{L = 2 \text{ mH}}$$

6.22. Given

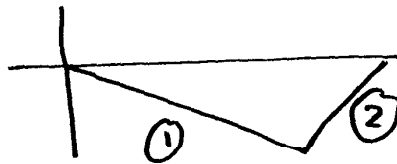


$$\text{in region ① } \frac{di}{dt} = \frac{-12 \text{ mA}}{4 \text{ ms}} = -3 \frac{\text{A}}{\text{s}}$$

$$\text{② } \frac{di}{dt} = \frac{12 \text{ mA}}{2 \text{ ms}} = 6 \frac{\text{A}}{\text{s}}$$

$$\text{① } v = L \frac{di}{dt} = (10 \times 10^{-3}) \cdot (-3) = -30 \text{ mV}$$
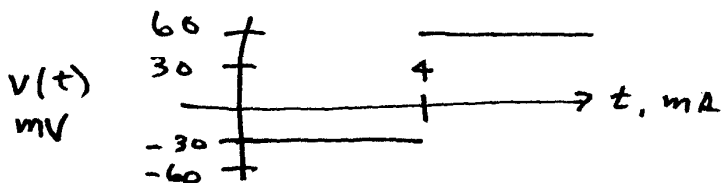
$$\text{② } v = L \frac{di}{dt} = (10 \times 10^{-3}) (6) = 60 \text{ mV}$$



6.23 There are 4 regions

$$\text{① } \frac{di}{dt} = 0$$


$$v = L \frac{di}{dt}$$

$$= (50 \times 10^{-3}) \frac{di}{dt} \text{ V}$$

$$\text{② } \frac{di}{dt} = \frac{-100 \text{ mA}}{2 \text{ ms}} = -50$$

$$\text{③ } \frac{di}{dt} = \frac{200 \text{ mA}}{4 \text{ ms}} = 50$$
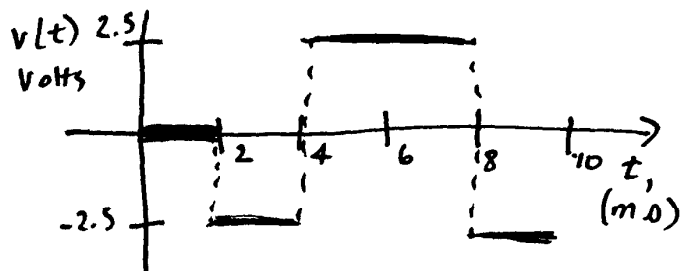
$$\text{④ } \frac{di}{dt} = \frac{-100 \text{ mA}}{2 \text{ ms}} = -50$$




6.47 We know an integrating opamp has $V_{out}(t) = -\frac{1}{RC} \int_{-\infty}^t V_{in}(x) dx$

here $R = 80 K\Omega$

We want $-\frac{1}{RC} = -10$, $C = \frac{1}{10R} = \underline{1.25 \mu F}$

6.48 $V_o = \int V_s dt - 10 V_s$

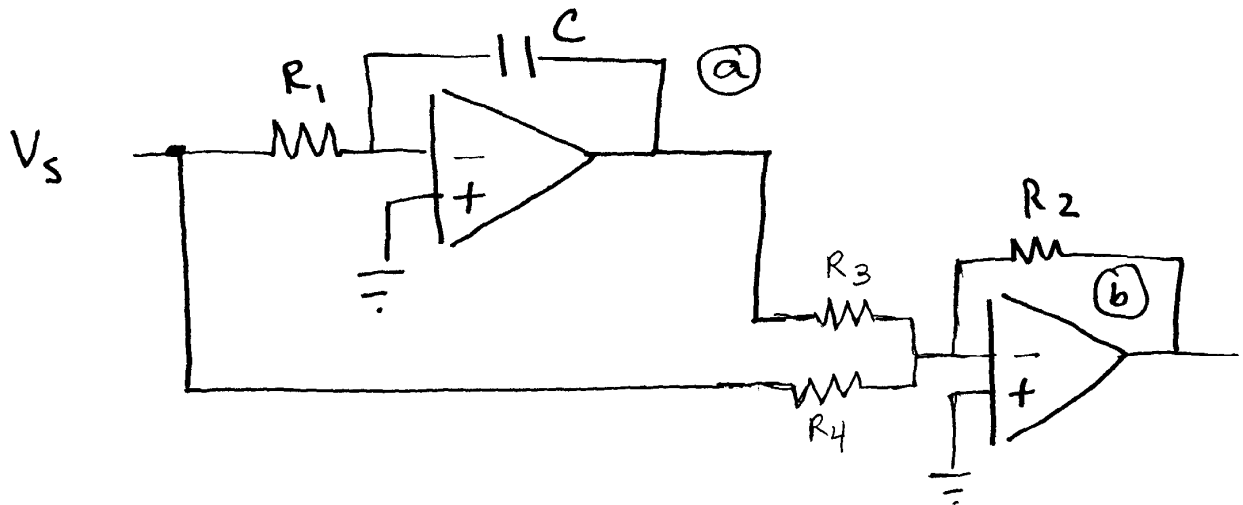

opamp (a) output = $-\frac{1}{RC} \int V_s dt$

choose $-\frac{1}{RC} = -1$ $RC = 1$ (e.g. $R_1 = 100 K\Omega$, $C = 10 \mu F$)

opamp (b) output = $-\left(\frac{R_3}{R_2}\right)\left(-\int V_s dt\right) - \left(\frac{R_4}{R_2}\right)V_s$

Choose $R_3 = R_2 = 10 K\Omega$

Choose $R_4 = 100 K\Omega$

output = $\int V_s dt - 10 V_s$